
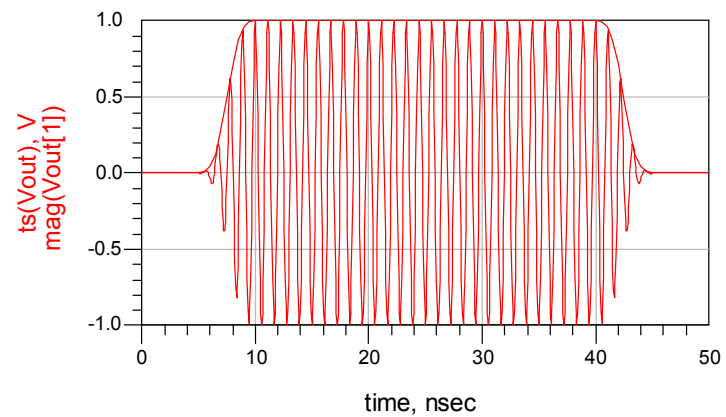
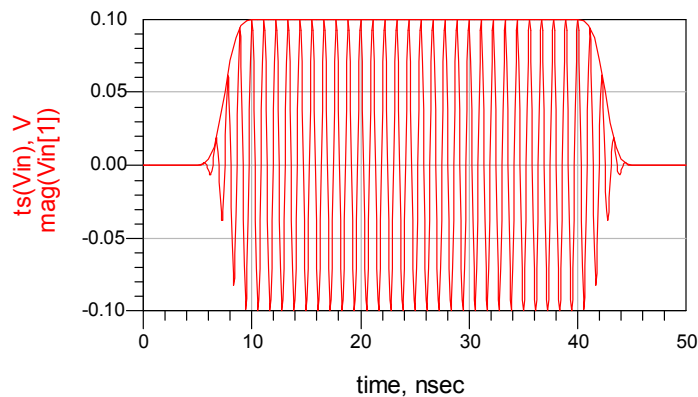


ADS Tutorial #5 Harmonic Balance and Envelop Simulation


Oklahoma State University





1. Envelop Simulation

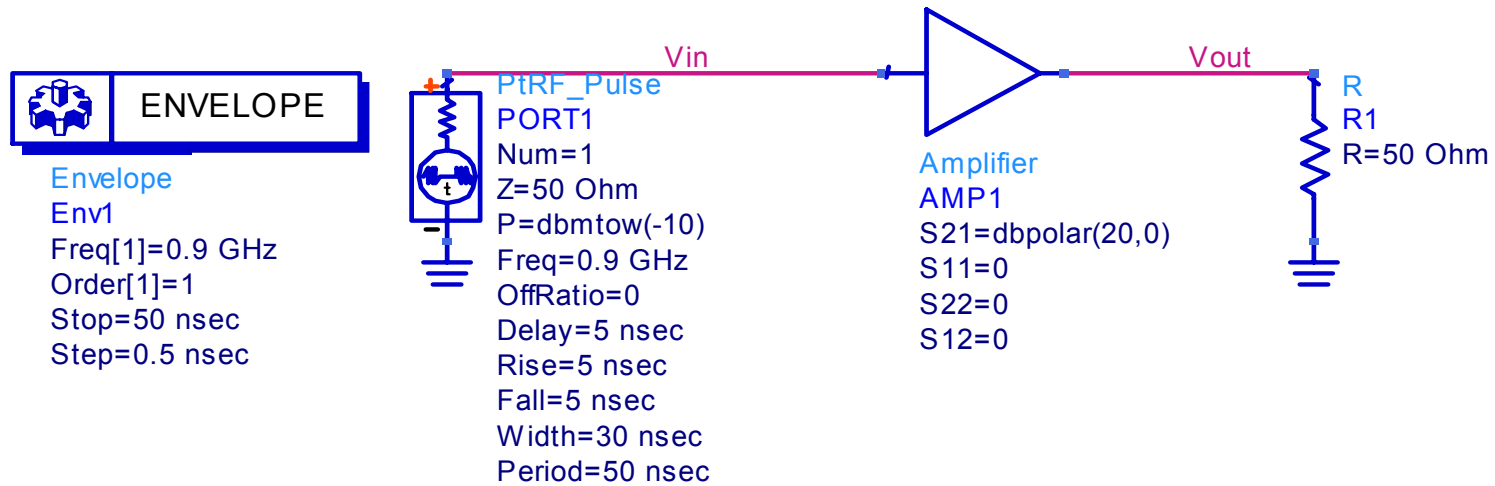

2. Harmonic Balance

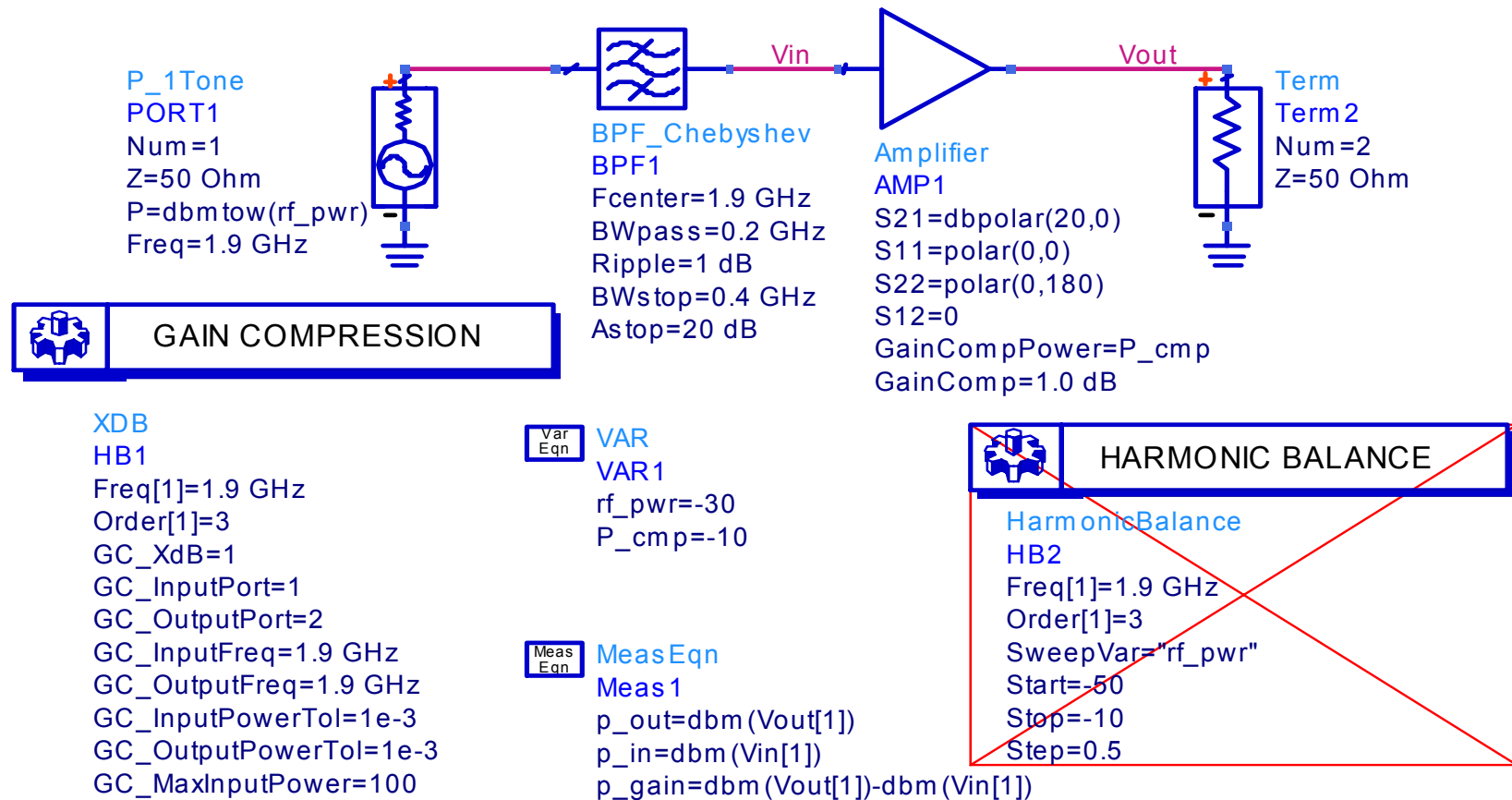1) System Level Amplifier (Gain Compression)



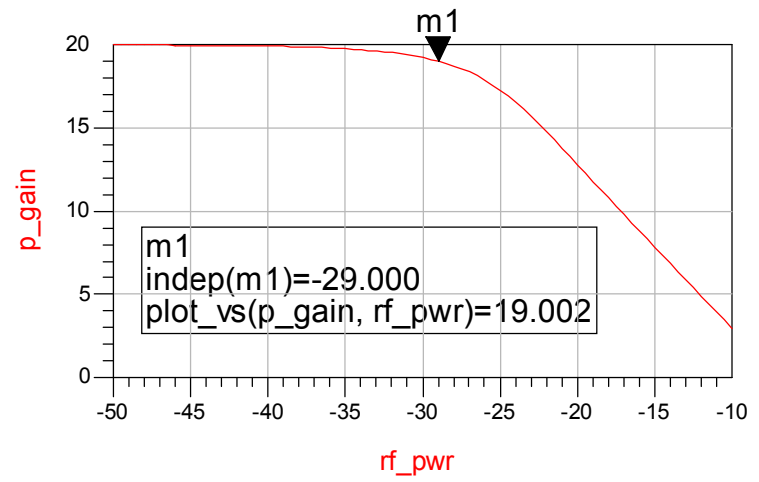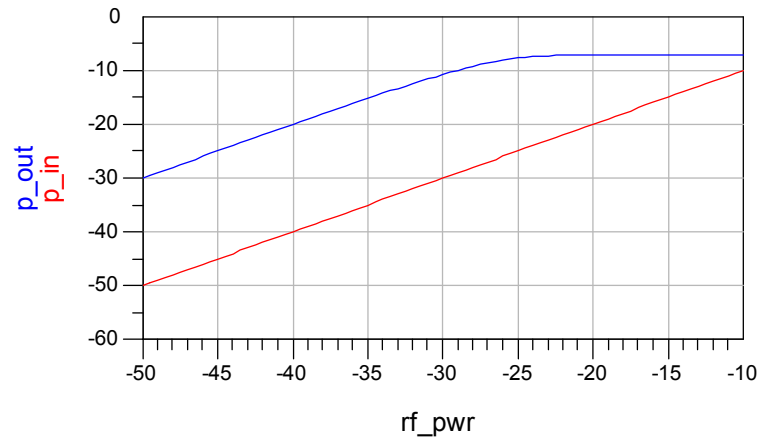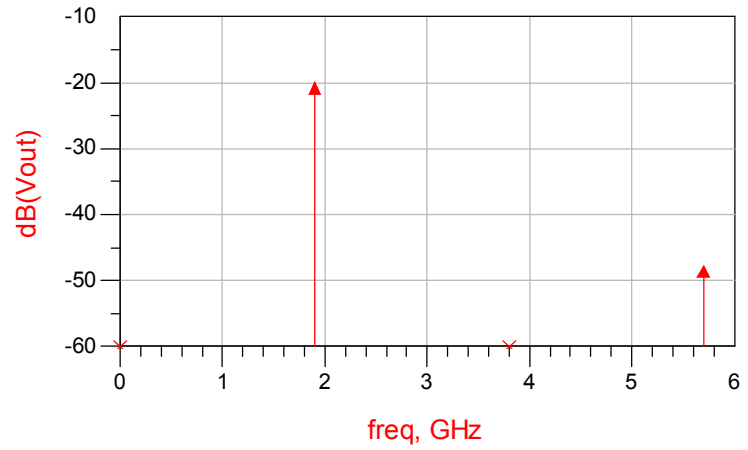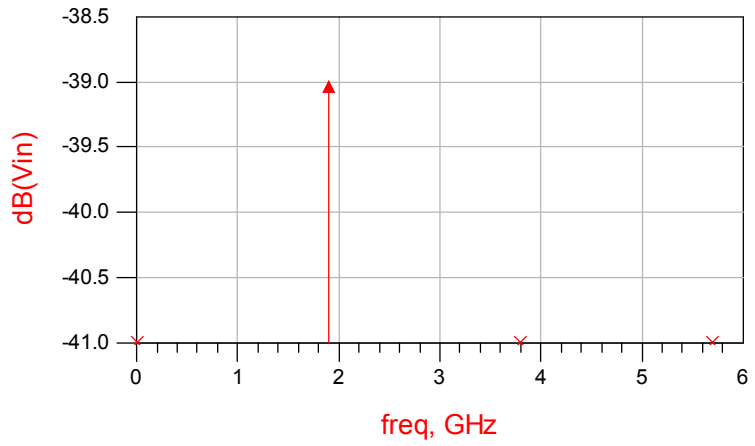




2) System Level Amplifier (Two-Tone)

 **HARMONIC BALANCE**

HarmonicBalance
 HB2
 MaxOrder=8
 Freq[1]=fc - f_hsp
 Freq[2]=fc + f_hsp
 Order[1]=4
 Order[2]=4

P_nTone
 PORT1
 Num=1
 Z=50 Ohm
 Freq[1]=fc - f_hsp
 Freq[2]=fc + f_hsp
 P[1]=dbmtow(rf_pwr)
 P[2]=dbmtow(rf_pwr)

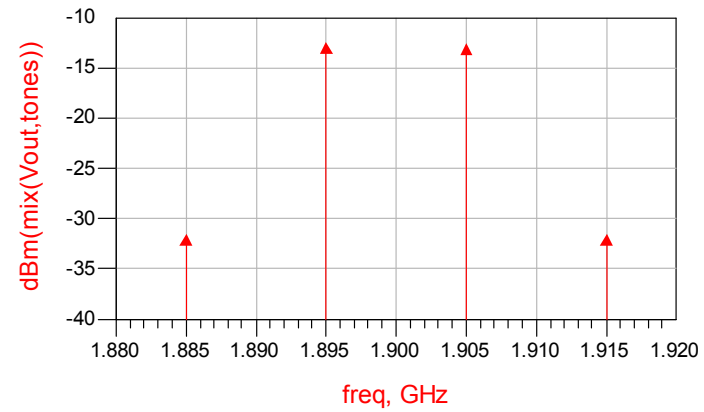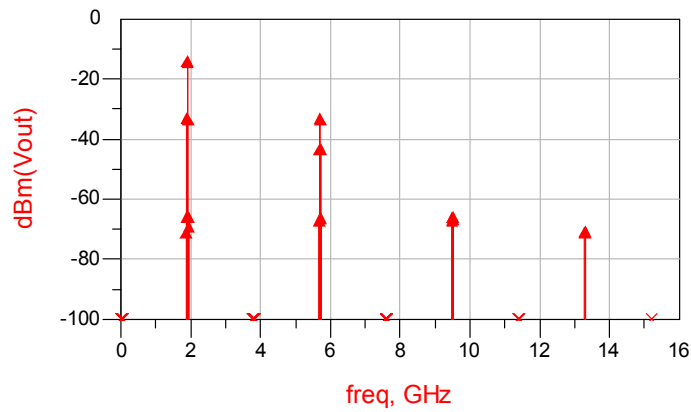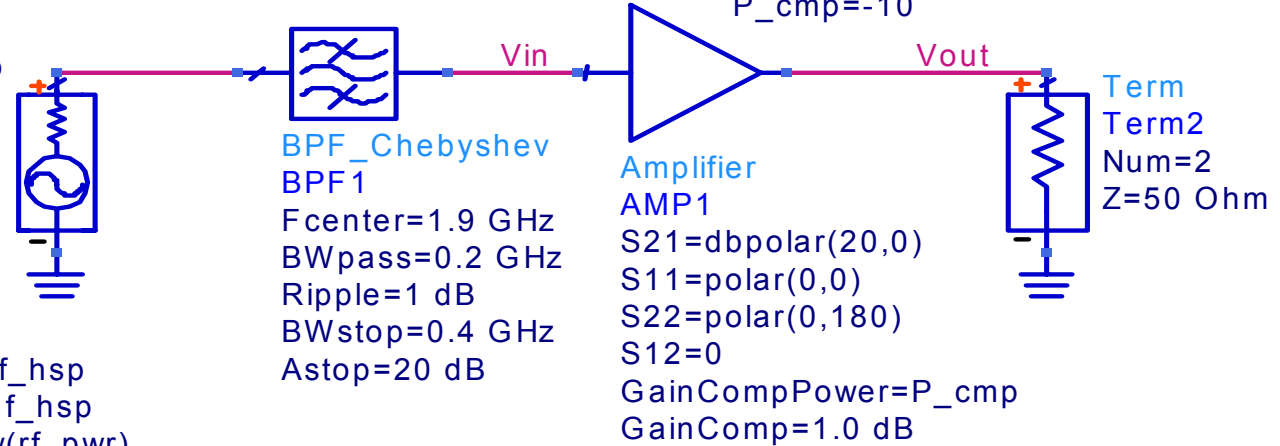Var Eqn
 VAR
 VAR1
 rf_pwr=-30
 fc=1.9 GHz
 f_hsp=5 MHz
 P_cmp=-10



3) BJT Amplifier (Harmonics and Waveforms)

Var Eqn
VAR
 VAR1
 RF_pwr=40
 Vbias=5 V


Meas Eqn
MeasEqn
 Meas1
 dbm_out=dBm(Vout)
 dbm_in=dBm(Vin)



GAIN COMPRESSION

XDB
 HB2
 Freq[1]=1.9 GHz
 Order[1]=3
 GC_XdB=1
 GC_InputPort=1
 GC_OutputPort=2
 GC_InputFreq=1.9 GHz
 GC_OutputFreq=1.9 GHz
 GC_InputPowerTol=1e-3
 GC_OutputPowerTol=1e-3
 GC_MaxInputPower=100

~~**HARMONIC BALANCE**~~

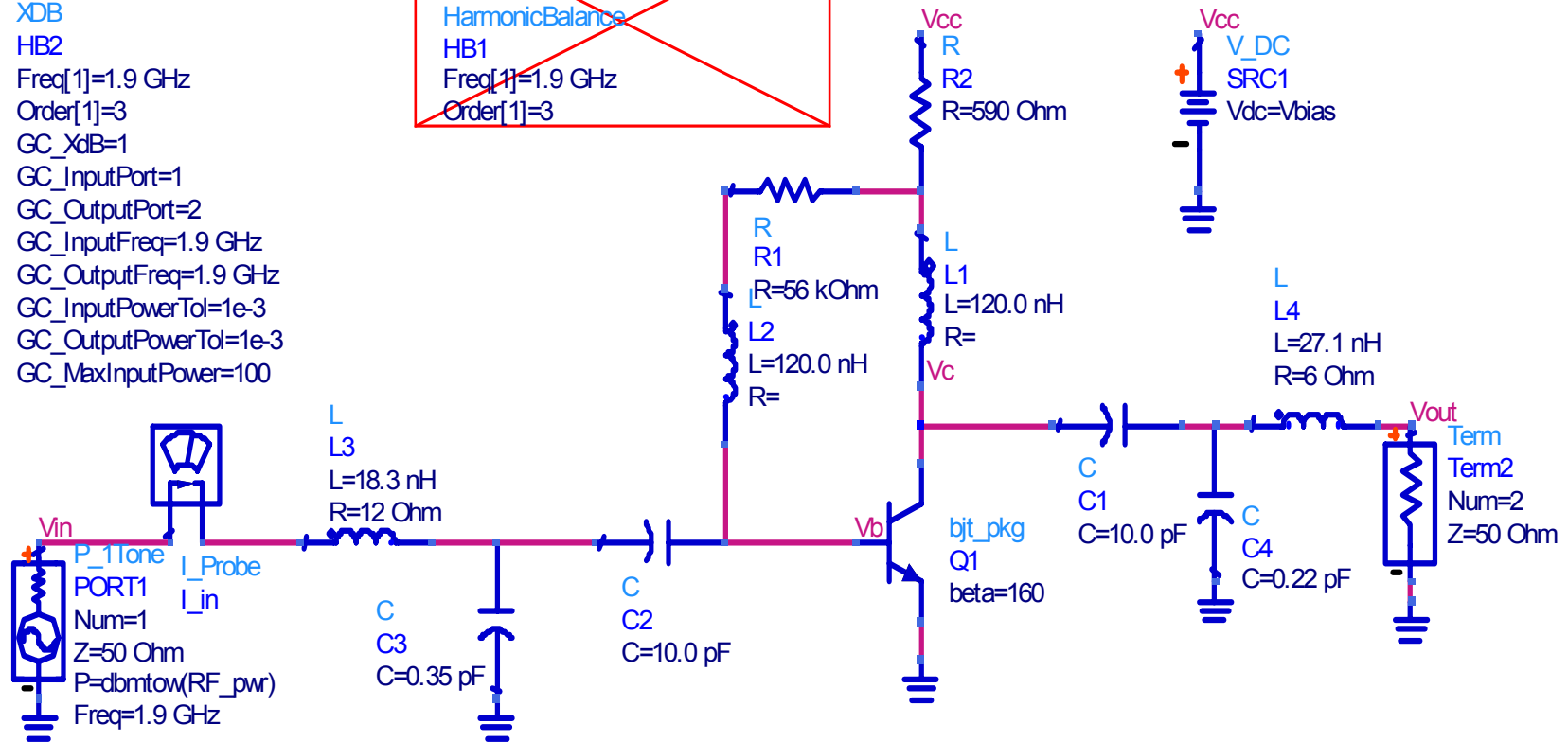~~HarmonicBalance
 HB1
 Freq[1]=1.9 GHz
 Order[1]=3~~



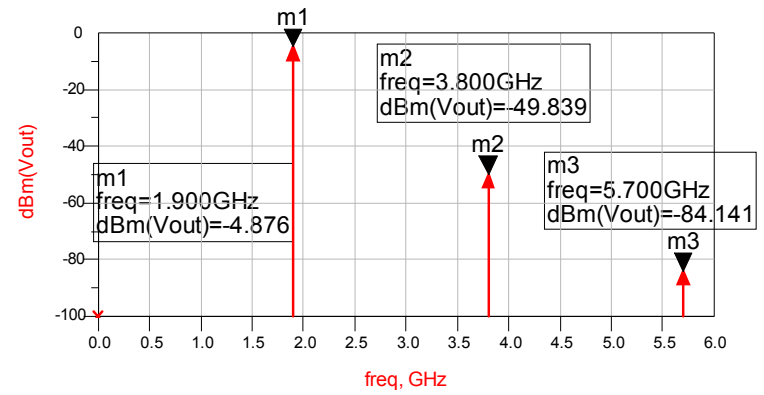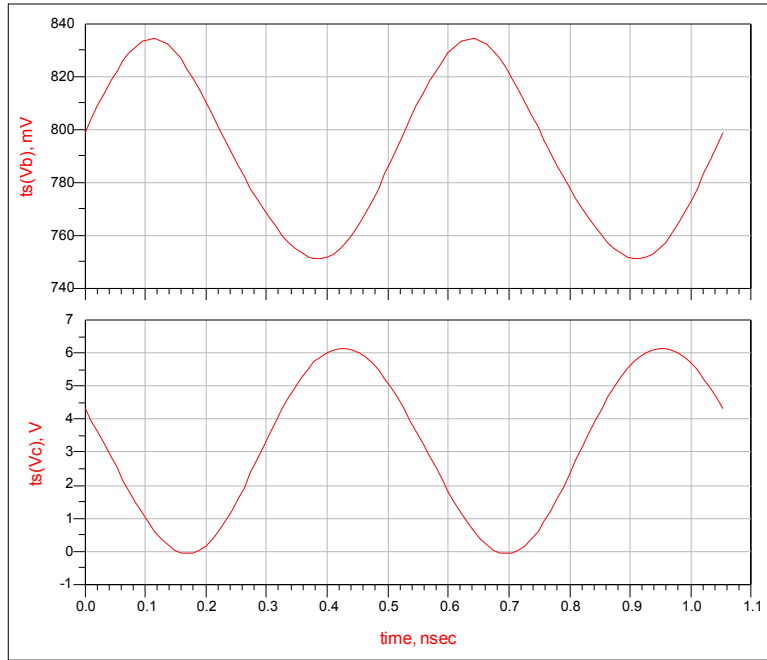

freq	inpwr	outpwr
0.0000 Hz	-30.67 dBm	3.498 dBm
1.900GHz	-30.67 dBm	3.498 dBm

4) BJT Amplifier (Gain Compression)

